

## Field Effect Transistors

### MEASURE THE CHARACTERISTICS OF A FIELD EFFECT TRANSISTOR

- Measure the drain current as a function of the drain-source voltage for various gate voltages.
- Confirm the shape of the characteristic when the drain current is governed by the drain-source voltage and the gate voltage.

UE3080300

06/16 UD

 


Fig. 1: Experiment set-up

### GENERAL PRINCIPLES

**A field effect transistor (FET) is a semiconductor component in which electric current passes through a channel and is controlled by an electric field acting perpendicular to the channel.**

FETs have three contacts, called source (S), drain (D) and gate (G) due to their respective functions. The channel comprises a conductive link between the source and the drain. If a voltage  $U_{DS}$  is applied between source and drain, a drain current  $I_D$  flows in the channel. The current is carried by carriers of only one polarity (unipolar transistors), i.e. electrons for an n-doped semiconductor channel and holes in a p-doped

channel. The cross-section or the conductivity of the channel is controlled by the electric field perpendicular to the channel. To create this field, a gate voltage  $U_{GS}$  is applied between the source and gate. The gate electrode is isolated from the channel by means of a reverse-biased pn junction or by an extra insulating layer (IGFET, MISFET, MOSFET). For insulated gate FETs the cross section of the channel is controlled by the expansion of the space-charge region of the junction, which is itself controlled by the perpendicular field.

In order to ensure that the pn junction is always reverse-biased, i.e. specifically to make sure that there is no current at the gate, the gate voltage  $U_{GS}$  and the drain-source voltage  $U_{DS}$  must meet the following condition for an n-channel FET

$$(1a) U_{GS} \leq 0, U_{DS} \geq 0$$

and the following for a p-channel FET

$$(1b) U_{GS} \geq 0, U_{DS} \geq 0.$$

If the absolute value of the drain-source voltage  $|U_{DS}|$  is small, the FET acts like an ohmic resistor with a correspondingly linear characteristic. As  $|U_{DS}|$  increases, the channel is restricted in size because the reverse-bias voltage between the gate and the channel increases in the direction of the drain. The space-charge region near the drain is wider than that near the source, meaning that the channel is narrower near the drain than it is near the source. At a specific voltage where  $U_{DS} = U_p$  the width of the channel becomes zero and the drain current no longer increases even though the drain-source voltage is increased. The characteristic passes out of its ohmic region into a region of saturation.

The extent of the space-charge region and therefore the size of the channel can be controlled by means of the gate voltage. As long as the gate voltage is non-zero, the channel can undergo additional constriction, making the drain-source current smaller and, in particular, the saturation current lower. The channel remains blocked irrespective of the drain-source voltage  $U_{DS}$  when  $|U_{GS}| \geq |U_p|$ .

The experiment involves measuring drain current  $I_D$  as a function of drain-source voltage  $U_{DS}$  for various gate voltages  $U_{GS}$ .

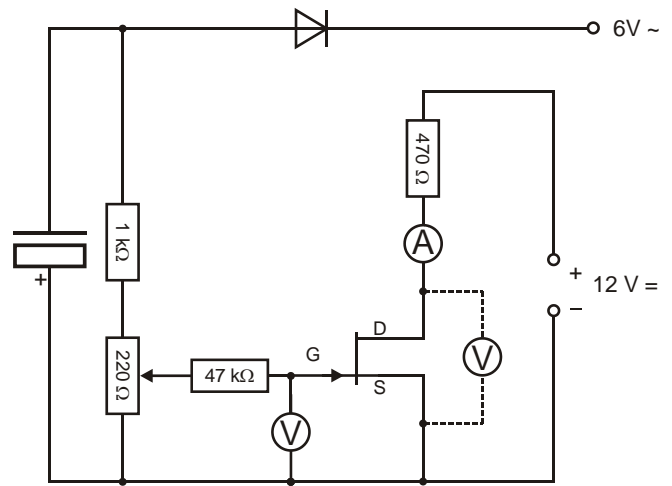


Fig. 2: Sketch of circuit.

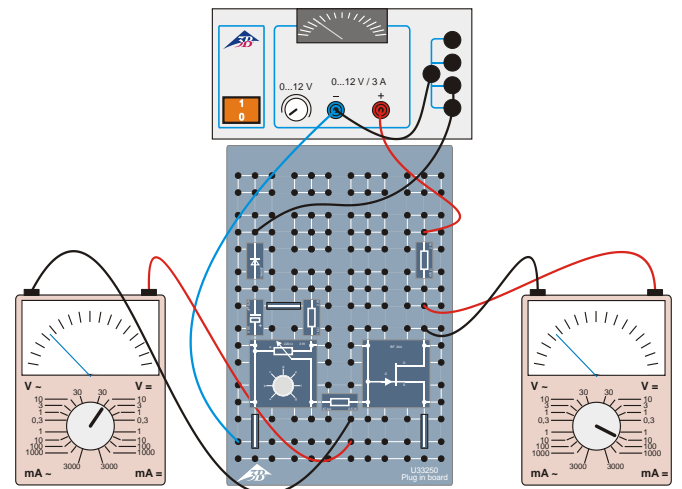


Fig. 3: Voltmeter between gate and source.

### LIST OF EQUIPMENT

1	Plug-In Board for Components	1012902 (U33250)
1	Set of 10 Jumpers, P2W19	1012985 (U333093)
1	Resistor, 1 kΩ, 2 W, P2W19	1012916 (U333024)
1	Resistor, 470 Ω, 2 W, P2W19	1012914 (U333022)
1	Resistor, 47 kΩ, 0,5 W, P2W19	1012926 (U333034)
1	Capacitor, 470 μF, 16 V, P2W19	1012960 (U333068)
1	FET Transistor, BF 244, P4W50	1012978 (U333086)
1	Silicon Diode, 1N 4007, P2W19	1012964 (U333072)
1	Potentiometer, 220 Ω, 3 W, P4W50	1012934 (U333042)
1	AC/DC Power Supply, 0...12 V/3 A @230 V	1002776 (U117601-230)
or		
1	AC/DC Power Supply, 0...12 V/3 A @115 V	1002775 (U117601-115)
2	Escola 30 Analogue Multimeter	1013526 (U8557330)
1	Set of 15 Experiment Leads, 75 cm, 1 mm <sup>2</sup>	1002840 (U13800)

### SET-UP AND EXPERIMENT PROCEDURE

- Set up the circuit as shown in Fig. 2 and Fig. 3. Make sure you get the correct polarity for the silicon diode and capacitor.
- Initially connect up the analogue multimeter so that you can measure the voltage between the gate and source. Connect the negative pole to the gate (Fig 3).
- Set up a measuring range of 10 V DC on the voltmeter and a range of 10 mA DC on the ammeter.
- Turn on the power supply and set the voltage to 0 V DC.
- Turn the potentiometer knob to position "a" to set up a gate voltage  $U_{GS}$  of 0 V.

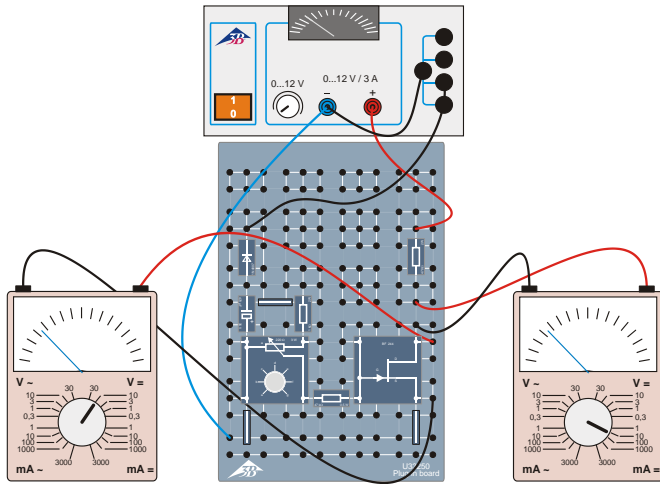


Fig. 4: Voltmeter between drain and source.

- Now connect the voltmeter between the drain and the source. Connect the positive pole to the drain (Fig. 4).
- Increase the voltage from the power supply until the drain-source voltage shown on the voltmeter is  $U_{DS} = 0.25 \text{ V}$ . Enter the value into Table 1.
- Read off the drain current  $I_D$  from the ammeter and enter the value into Table 1.
- Set up a drain-source voltage  $U_{DS} = 0.5 \text{ V}$  and enter the value into Table 1.
- Read off the drain current  $I_D$  from the ammeter and enter the value into Table 1.
- Increase the drain-source voltage  $U_{DS}$  in steps of  $0.5 \text{ V}$ . For each step, read off the drain current  $I_D$  from the ammeter and enter the values into Table 1.
- Turn the voltage back to  $0 \text{ V}$  on the power supply.
- Set up gate voltages  $U_{GS} = -0.5 \text{ V}$ ,  $-1 \text{ V}$  and  $-1.5 \text{ V}$ , repeat the above set of measurements for each of these voltages, then enter the drain-source voltages and corresponding drain currents into Table 1.

### SAMPLE MEASUREMENT

Table 1: Configured drain-source voltages with corresponding measurements of drain current for various gate voltages.

$U_{DS} / \text{V}$	$I_D / \text{mA}$			
	$U_{GS} = 0.0 \text{ V}$	$U_{GS} = -0.5 \text{ V}$	$U_{GS} = -1.0 \text{ V}$	$U_{GS} = -1.5 \text{ V}$
0.00	0.00	0.00	0.00	0.00
0.25	1.20	0.90	0.65	0.40
0.50	2.40	1.90	1.35	0.80
1.00	4.30	3.40	2.30	1.25
1.50	5.70	4.20	2.70	1.45
2.00	6.50	4.60	2.95	1.50
2.50	6.90	4.90	3.05	1.55
3.00	7.10	5.00	3.15	1.60
3.50	7.30	5.10	3.20	1.65
4.00	7.40	5.15	3.25	1.65
4.50	7.45	5.20	3.30	1.65
5.00	7.50	5.25	3.30	1.65

### EVALUATION

- Plot a graph of  $I_D$  against  $U_{DS}$  for each of the various gate voltages (Fig. 5)

The expected shape of the characteristics arising from controlling the drain current by means of the drain-source voltage and gate voltage is confirmed to be as described.

 


Fig. 5: Characteristic curves for a field effect transistor at various gate voltages.

